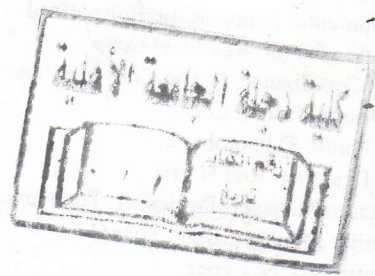


Seventh Edition

DIGITAL FUNDAMENTALS

Thomas L. Floyd



Prentice Hall International, Inc.

CONTENTS

1 **INTRODUCTORY DIGITAL CONCEPTS** 1

- 1-1 Digital and Analog Quantities 2
- 1-2 Binary Digits, Logic Levels, and Digital Waveforms 4
- 1-3 Basic Logic Operations 11
- 1-4 Basic Logic Functions 13
- 1-5 Digital Integrated Circuits 18
- 1-6 Testing and Troubleshooting Instruments 22
- 1-7 Digital System Application 30

2 **NUMBER SYSTEMS, OPERATIONS, AND CODES** 38

- 2-1 Decimal Numbers 40
- 2-2 Binary Numbers 41
- 2-3 Decimal-to-Binary Conversion 45
- 2-4 Binary Arithmetic 48
- 2-5 1's and 2's Complements of Binary Numbers 51
- 2-6 Signed Numbers 53
- 2-7 Arithmetic Operations with Signed Numbers 59
- 2-8 Hexadecimal Numbers 65
- 2-9 Octal Numbers 71
- 2-10 Binary Coded Decimal (BCD) 74
- 2-11 Digital Codes and Parity 76
- 2-12 Digital System Application 85

3 **LOGIC GATES** 98

- 3-1 The Inverter 100
- 3-2 The AND Gate 103
- 3-3 The OR Gate 109
- 3-4 The NAND Gate 114
- 3-5 The NOR Gate 119
- 3-6 The Exclusive-OR and Exclusive-NOR Gates 123
- 3-7 Integrated Circuit Logic Gates 127
- 3-8 Troubleshooting 138
- 3-9 Digital System Application 144

4 BOOLEAN ALGEBRA AND LOGIC SIMPLIFICATION 162

- 4-1 Boolean Operations and Expressions 164
- 4-2 Laws and Rules of Boolean Algebra 165
- 4-3 DeMorgan's Theorems 170
- 4-4 Boolean Analysis of Logic Circuits 174
- 4-5 Simplification Using Boolean Algebra 176
- 4-6 Standard Forms of Boolean Expressions 179
- 4-7 Boolean Expressions and Truth Tables 185
- 4-8 The Karnaugh Map 188
- 4-9 Karnaugh Map SOP Minimization 191
- 4-10 Karnaugh Map POS Minimization 200
- 4-11 Five-Variable Karnaugh Maps 204
- 4-12 Digital System Application 206

5 COMBINATIONAL LOGIC 224

- 5-1 Basic Combinational Logic Circuits 226
- 5-2 Implementing Combinational Logic 231
- 5-3 The Universal Property of NAND and NOR Gates 237
- 5-4 Combinational Logic Using NAND and NOR Gates 239
- 5-5 Operation with Pulse Waveforms 244
- 5-6 Troubleshooting 248
- 5-7 Digital System Application 254

6 FUNCTIONS OF COMBINATIONAL LOGIC 270

- 6-1 Basic Adders 272
- 6-2 Parallel Binary Adders 275
- 6-3 Comparators 283
- 6-4 Decoders 287
- 6-5 Encoders 296
- 6-6 Code Converters 300
- 6-7 Multiplexers (Data Selectors) 304
- 6-8 Demultiplexers 312
- 6-9 Parity Generators/Checkers 314
- 6-10 Troubleshooting 317
- 6-11 Digital System Application 320

7 INTRODUCTION TO PROGRAMMABLE LOGIC DEVICES 344

- 7-1 PLD Arrays and Classifications 346
- 7-2 Programmable Array Logic (PAL) 348
- 7-3 Generic Array Logic (GAL) 354

- 7-4 The GAL22V10 357
- 7-5 The GAL16V8 365
- 7-6 PLD Programming 368
- 7-7 PLD Software 371
- 7-8 Digital System Application 380

8 FLIP-FLOPS AND RELATED DEVICES 392

- 8-1 Latches 394
- 8-2 Edge-Triggered Flip-Flops 400
- 8-3 Master-Slave Flip-Flops 411
- 8-4 Flip-Flop Operating Characteristics 414
- 8-5 Flip-Flop Applications 417
- 8-6 One-Shots 421
- 8-7 The 555 Timer 427
- 8-8 Troubleshooting 432
- 8-9 Digital System Application 435

9 COUNTERS 452

- 9-1 Asynchronous Counter Operation 454
- 9-2 Synchronous Counter Operation 462
- 9-3 Up/Down Synchronous Counters 469
- 9-4 Design of Synchronous Counters 473
- 9-5 Cascaded Counters 482
- 9-6 Counter Decoding 486
- 9-7 Counter Applications 490
- 9-8 Troubleshooting 494
- 9-9 Logic Symbols with Dependency Notation 499
- 9-10 Digital System Application 500

10 SHIFT REGISTERS 520

- 10-1 Basic Shift Register Functions 522
- 10-2 Serial In/Serial Out Shift Registers 523
- 10-3 Serial In/Parallel Out Shift Registers 527
- 10-4 Parallel In/Serial Out Shift Registers 529
- 10-5 Parallel In/Parallel Out Shift Registers 532
- 10-6 Bidirectional Shift Registers 534
- 10-7 Shift Register Counters 537
- 10-8 Shift Register Applications 541
- 10-9 Troubleshooting 547
- 10-10 Logic Symbols with Dependency Notation 549
- 10-11 Digital System Application 551

11 SEQUENTIAL LOGIC APPLICATIONS OF PLDS 568

- 11-1 The Complete OLMC 570
- 11-2 OLMC Mode Selection 573
- 11-3 Implementing Shift Registers with PLDs 577
- 11-4 Implementing Counters with PLDs 581
- 11-5 PLD System Implementation 589
- 11-6 Digital System Application 599

12 MEMORY AND STORAGE 610

- 12-1 Basics of Semiconductor Memory 612
- 12-2 Random-Access Memories (RAMs) 615
- 12-3 Read-Only Memories (ROMs) 629
- 12-4 Programmable ROMs (PROMs and EPROMs) 634
- 12-5 Flash Memories 638
- 12-6 Memory Expansion 642
- 12-7 Special Types of Memories 648
- 12-8 Magnetic and Optical Storage 654
- 12-9 Testing and Troubleshooting 660
- 12-10 Digital System Application 664

13 INTERFACING 682

- 13-1 Digital and Analog Interfacing 684
- 13-2 Digital-to-Analog (D/A) Conversion 687
- 13-3 Analog-to-Digital (A/D) Conversion 694
- 13-4 Troubleshooting DACs and ADCs 704
- 13-5 Internal System Interfacing 708
- 13-6 Standard Buses 712
- 13-7 Digital System Application 722

14 INTRODUCTION TO MICROPROCESSORS AND COMPUTERS 740

- 14-1 The Microprocessor and the Computer 742
- 14-2 Microprocessor Families 747
- 14-3 The 8086/8088 Microprocessor and Software Model for the Pentium Processor 751
- 14-4 Microprocessor Programming 758
- 14-5 The Central Processing Unit (CPU) 765
- 14-6 The Memory 770
- 14-7 The Input/Output (I/O) Port 774
- 14-8 Interrupts 777
- 14-9 Direct Memory Access (DMA) 779

15 INTEGRATED CIRCUIT TECHNOLOGIES 788

- 15-1 Basic Operational Characteristics and Parameters 790
- 15-2 CMOS Circuits 798
- 15-3 TTL Circuits 803
- 15-4 Practical Considerations in the Use of TTL 808
- 15-5 Comparison of CMOS and TTL Performance 816
- 15-6 Emitter-Coupled Logic (ECL) Circuits 817
- 15-7 PMOS, NMOS, and E²CMOS 818

Appendix A
DATA SHEETS A-1

Appendix B
CONVERSIONS A-48

Answers to Selected Odd-Numbered Problems A-50

Glossary GL-1

Index IN-1