

Computer SYSTEM architecture

THIRD edition

M. MORRIS MANO

SECTION 1-7 Sequential Circuits 29

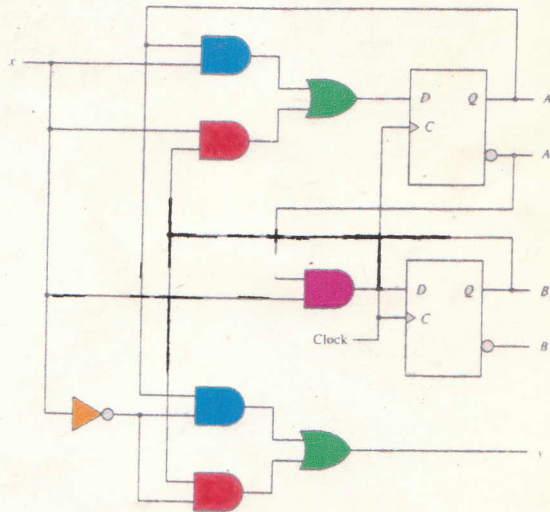


Figure 1-25 Example of a sequential circuit.

Contents

Preface

xv

CHAPTER ONE

Digital Logic Circuits

		1
1-1	Digital Computers	1
1-2	Logic Gates	4
1-3	Boolean Algebra	7
	Complement of a Function	10
1-4	Map Simplification	11
	Product-of-Sums Simplification	14
	Don't-Care Conditions	16
1-5	Combinational Circuits	18
	Half-Adder	19
	Full-Adder	20
1-6	Flip-Flops	22
	SR Flip-Flop	22
	D Flip-Flop	23
	JK Flip-Flop	24
	T Flip-Flop	24
	Edge-Triggered Flip-Flops	25
	Excitation Tables	27
1-7	Sequential Circuits	28
	Flip-Flop Input Equations	28
	State Table	30
	State Diagram	31
	Design Example	32
	Design Procedure	36
	Problems	37
	References	39

CHAPTER TWO
Digital Components

		41
2-1	Integrated Circuits	41
2-2	Decoders	43
	NAND Gate Decoder	45
	Decoder Expansion	46
	Encoders	47
2-3	Multiplexers	48
2-4	Registers	50
	Register with Parallel Load	51
2-5	Shift Registers	53
	Bidirectional Shift Register with Parallel Load	53
2-6	Binary Counters	56
	Binary Counter with Parallel Load	58
2-7	Memory Unit	58
	Random-Access Memory	60
	Read-Only Memory	61
	Types of ROMs	62
	Problems	63
	References	65

CHAPTER THREE
Data Representation

		67
3-1	Data Types	67
	Number Systems	68
	Octal and Hexadecimal Numbers	69
	Decimal Representation	72
	Alphanumeric Representation	73
3-2	Complements	74
	($r-1$)'s Complement	75
	(r)'s Complement	75
	Subtraction of Unsigned Numbers	76
3-3	Fixed-Point Representation	77
	Integer Representation	78
	Arithmetic Addition	79
	Arithmetic Subtraction	80
	Overflow	80
	Decimal Fixed-Point Representation	81

3-4	Floating-Point Representation	83
3-5	Other Binary Codes	84
	Gray Code	84
	Other Decimal Codes	85
	Other Alphanumeric Codes	86
3-6	Error Detection Codes	87
	Problems	89
	References	91

CHAPTER FOUR

	Register Transfer and Microoperations	93
4-1	Register Transfer Language	93
4-2	Register Transfer	95
4-3	Bus and Memory Transfers	97
	Three-State Bus Buffers	100
	Memory Transfer	101
4-4	Arithmetic Microoperations	102
	Binary Adder	103
	Binary Adder-Subtractor	104
	Binary Incrementer	105
	Arithmetic Circuit	106
4-5	Logic Microoperations	108
	List of Logic Microoperations	109
	Hardware Implementation	111
	Some Applications	111
4-6	Shift Microoperations	114
	Hardware Implementation	115
4-7	Arithmetic Logic Shift Unit	116
	Problems	119
	References	122

CHAPTER FIVE

	Basic Computer Organization and Design	123
5-1	Instruction Codes	123
	Stored Program Organization	125
	Indirect Address	126

5-2	Computer Registers	127
	Common Bus System	129
5-3	Computer Instructions	132
	Instruction Set Completeness	134
5-4	Timing and Control	135
5-5	Instruction Cycle	139
	Fetch and Decode	139
	Determine the Type of Instruction	141
	Register-Reference Instructions	143
5-6	Memory-Reference Instructions	145
	AND to AC	145
	ADD to AC	146
	LDA: Load to AC	146
	STA: Store AC	147
	BUN: Branch Unconditionally	147
	BSA: Branch and Save Return Address	147
	ISZ: Increment and Skip If Zero	149
	Control Flowchart	149
5-7	Input-Output and Interrupt	150
	Input-Output Configuration	151
	Input-Output Instructions	152
	Program Interrupt	153
	Interrupt Cycle	156
5-8	Complete Computer Description	157
5-9	Design of Basic Computer	157
	Control Logic Gates	160
	Control of Registers and Memory	160
	Control of Single Flip-Flops	162
	Control of Common Bus	162
5-10	Design of Accumulator Logic	164
	Control of AC Register	165
	Adder and Logic Circuit	166
	Problems	167
	References	171

CHAPTER SIX

	Programming the Basic Computer	173
6-1	Introduction	173
6-2	Machine Language	174

6-3	Assembly Language	179
	Rules of the Language	179
	An Example	181
	Translation to Binary	182
6-4	The Assembler	183
	Representation of Symbolic Program	
	in Memory	184
	First Pass	185
	Second Pass	187
6-5	Program Loops	190
6-6	Programming Arithmetic and Logic	
	Operations	192
	Multiplication Program	193
	Double-Precision Addition	196
	Logic Operations	197
	Shift Operations	197
6-7	Subroutines	198
	Subroutines Parameters and Data Linkage	200
6-8	Input-Output Programming	203
	Character Manipulation	204
	Program Interrupt	205
	Problems	208
	References	211

CHAPTER SEVEN

Microprogrammed Control 213

7-1	Control Memory	213
7-2	Address Sequencing	216
	Conditional Branching	217
	Mapping of Instruction	219
	Subroutines	220
7-3	Microprogram Example	220
	Computer Configuration	220
	Microinstruction Format	222
	Symbolic Microinstructions	225
	The Fetch Routine	226
	Symbolic Microprogram	227
	Binary Microprogram	229

7-4	Design of Control Unit	231
	Microprogram Sequencer	232
	Problems	235
	References	238

CHAPTER EIGHT

Central Processing Unit

8-1	Introduction	241
8-2	General Register Organization	242
	Control Word	244
	Examples of Microoperations	246
8-3	Stack Organization	247
	Register Stack	247
	Memory Stack	249
	Reverse Polish Notation	251
	Evaluation of Arithmetic Expressions	253
8-4	Instruction Formats	255
	Three-Address Instructions	258
	Two-Address Instructions	258
	One-Address Instructions	259
	Zero-Address Instructions	259
	RISC Instructions	259
8-5	Addressing Modes	260
	Numerical Example	264
8-6	Data Transfer and Manipulation	266
	Data Transfer Instructions	267
	Data Manipulation Instructions	268
	Arithmetic Instructions	269
	Logical and Bit Manipulation Instructions	270
	Shift Instructions	271
8-7	Program Control	273
	Status Bit Conditions	274
	Conditional Branch Instructions	275
	Subroutine Call and Return	278
	Program Interrupt	279
	Types of Interrupts	281
8-8	Reduced Instruction Set Computer (RISC)	282
	CISC Characteristics	283
	RISC Characteristics	284

Overlapped Register Windows	285	
Berkeley RISC I	288	
Problems		291
References		297

CHAPTER NINE

Pipeline and Vector Processing 299

9-1	Parallel Processing		299
9-2	Pipelining		302
	General Considerations	304	
9-3	Arithmetic Pipeline		307
9-4	Instruction Pipeline		310
	Example: Four-Segment Instruction Pipeline	311	
	Data Dependency	313	
	Handling of Branch Instructions	314	
9-5	RISC Pipeline		315
	Example: Three-Segment Instruction Pipeline	316	
	Delayed Load	317	
	Delayed Branch	318	
9-6	Vector Processing		319
	Vector Operations	321	
	Matrix Multiplication	322	
	Memory Interleaving	324	
	Supercomputers	325	
9-7	Array Processors		326
	Attached Array Processor	326	
	SIMD Array Processor	327	
	Problems		329
	References		330

CHAPTER TEN

Computer Arithmetic 333

10-1	Introduction	333
10-2	Addition and Subtraction	334
	Addition and Subtraction with Signed-Magnitude Data	335

	Hardware Implementation	336	
	Hardware Algorithm	337	
	Addition and Subtraction with Signed-2's Complement Data	338	
10-3	Multiplication Algorithms		340
	Hardware Implementation for Signed-Magnitude Data	341	
	Hardware Algorithm	342	
	Booth Multiplication Algorithm	343	
	Array Multiplier	346	
10-4	Division Algorithms		348
	Hardware Implementation for Signed-Magnitude Data	349	
	Divide Overflow	351	
	Hardware Algorithm	352	
	Other Algorithms	353	
10-5	Floating-Point Arithmetic Operations		354
	Basic Considerations	354	
	Register Configuration	357	
	Addition and Subtraction	358	
	Multiplication	360	
	Division	362	
10-6	Decimal Arithmetic Unit		363
	BCD Adder	365	
	BCD Subtraction	368	
10-7	Decimal Arithmetic Operations		369
	Addition and Subtraction	371	
	Multiplication	371	
	Division	374	
	Floating-Point Operations	376	
	Problems		376
	References		380

CHAPTER ELEVEN

	Input-Output Organization		381
11-1	Peripheral Devices		381
	ASCII Alphanumeric Characters	383	
11-2	Input-Output Interface		385
	I/O Bus and Interface Modules	386	
	I/O versus Memory Bus	387	

	Isolated versus Memory-Mapped I/O	388
	Example of I/O Interface	389
11-3	Asynchronous Data Transfer	391
	Strobe Control	391
	Handshaking	393
	Asynchronous Serial Transfer	396
	Asynchronous Communication Interface	398
	First-In, First-Out Buffer	400
11-4	Modes of Transfer	402
	Example of Programmed I/O	403
	Interrupt-Initiated I/O	406
	Software Considerations	406
11-5	Priority Interrupt	407
	Daisy-Chaining Priority	408
	Parallel Priority Interrupt	409
	Priority Encoder	411
	Interrupt Cycle	412
	Software Routines	413
	Initial and Final Operations	414
11-6	Direct Memory Access (DMA)	415
	DMA Controller	416
	DMA Transfer	418
11-7	Input-Output Processor (IOP)	420
	CPU-IOP Communication	422
	IBM 370 I/O Channel	423
	Intel 8089 IOP	427
11-8	Serial Communication	429
	Character-Oriented Protocol	432
	Transmission Example	433
	Data Transparency	436
	Bit-Oriented Protocol	437
	Problems	439
	References	442

CHAPTER TWELVE

Memory Organization 445

12-1	Memory Hierarchy	445
12-2	Main Memory	448
	RAM and ROM Chips	449